

If  $a\%5 = \alpha$  and  $b\%5 = \beta$  then  $(a + b)\%5 = (\alpha + \beta)\%5$ .

$$3\%5 = 3$$

$$6\%5 = 1$$

$$(3+6)\%5 = 9\%5 = 4$$

$$(3+1)\%5 = 4\%5 = 4$$

If a current string has a numerical value of  $x$ ,

=> placing a 0 on the right hand side results in a string having a value of  $x+x$

Example =  $1010 = 10$   
 $10100 = 20$

=> placing a 1 results in a string having a value  $x+x+1$

Example =  $1010 = 10$   
 $10101 = 21$

Possible remainder: 0, 1, 2, 3, or 4

Five possible states

Each state number indicates the remainder


Start state is 000 and final state is 000 because remainder of 0 means that number is divisible by 5

	input	output
=> state (000) <i>Remainder = 0</i>		
-> if next input is 00, (0), $0 \bmod 5 = 0$	0	true = 1 on logism
-> if next input is 01, (1), $1 \bmod 5 = 1$	1	false = 0 on logism
 => state (001) <i>Remainder = 1</i>		
-> if next input is 10, (2), $2 \bmod 5 = 2$	0	
-> if next input is 11, (3), $3 \bmod 5 = 3$	1	
 => state (010) <i>Remainder = 2</i>		
-> if next input is 100, (4), $4 \bmod 5 = 4$	0	
-> if next input is 101, (5), $5 \bmod 5 = 0$	1	
 => state (011) <i>Remainder = 3</i>		
-> if next input is 110, (6), $6 \bmod 5 = 1$	0	
-> if next input is 111, (7), $7 \bmod 5 = 2$	1	
 => state (100) <i>Remainder = 4</i>		
-> if next input is 1000, (8), $8 \bmod 5 = 3$	0	
-> if next input is 1001, (9), $9 \bmod 5 = 4$	1	

## Symbolic state transition table

State	Input	next state	output
Remainder = 0	0	Remainder = 0	True
	1	Remainder = 1	True
Remainder = 1	0	Remainder = 2	False
	1	Remainder = 3	False
Remainder = 2	0	Remainder = 4	False
	1	Remainder = 0	False
Remainder = 3	0	Remainder = 1	False
	1	Remainder = 2	False
Remainder = 4	0	Remainder = 3	False
	1	Remainder = 4	False

## Finite state machine diagram

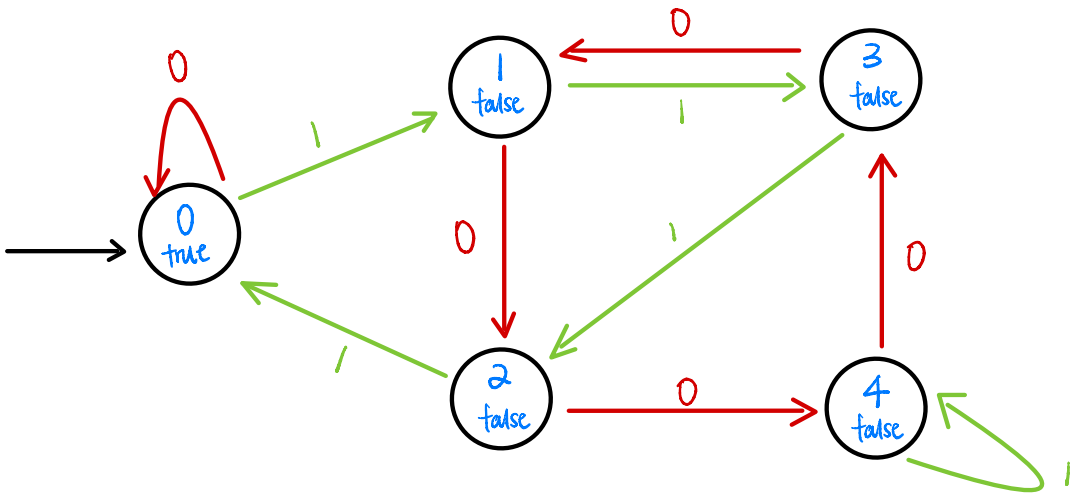

# True Table

Encoded state transition table  
D flip-flop

	$S_2$	$S_1$	$S_0$	$\bar{i}$	$S_2'$	$S_1'$	$S_0'$	output	$D_2$	$D_1$	$D_0$
0	0	0	0	0	0	0	0	1	0	0	0
	0	0	0	1	0	0	1	1	0	0	1
1	0	0	1	0	0	1	0	0	0	1	0
	0	0	1	1	0	1	1	0	0	1	1
2	0	1	0	0	1	0	0	0	1	0	0
	0	1	0	1	0	0	0	0	0	0	0
3	0	1	1	0	0	0	1	0	0	0	1
	0	1	1	1	0	1	0	0	0	1	0
4	1	0	0	0	0	1	1	0	0	1	1
	1	0	0	1	1	0	0	0	1	0	0

## Expressions

$$\text{output} = \bar{S}_2 \cdot \bar{S}_1 \cdot \bar{S}_0$$

$$D_2 = S_2' = \bar{S}_2 \cdot S_1 \cdot \bar{S}_0 \cdot \bar{i} + S_2 \cdot \bar{S}_1 \cdot \bar{S}_0 \cdot i$$

$$\begin{aligned} D_1 = S_1' &= \bar{S}_2 \cdot \bar{S}_1 \cdot S_0 \cdot i + \bar{S}_2 \cdot \bar{S}_1 \cdot S_0 \cdot \bar{i} + \bar{S}_2 \cdot S_1 \cdot S_0 \cdot i + S_2 \cdot \bar{S}_1 \cdot \bar{S}_0 \cdot \bar{i} \\ &= \bar{S}_2 \cdot S_0 \cdot i (\bar{S}_1 + S_1) + \bar{S}_1 \cdot \bar{i} (\bar{S}_2 \cdot S_0 + S_2 \cdot \bar{S}_0) \\ &= \bar{S}_2 \cdot S_0 \cdot i + \bar{S}_1 \cdot \bar{i} (\bar{S}_2 \cdot S_0 + S_2 \cdot \bar{S}_0) \end{aligned}$$

$$\begin{aligned} D_0 = S_0' &= \bar{S}_2 \cdot \bar{S}_1 \cdot \bar{S}_0 \cdot i + \bar{S}_2 \cdot \bar{S}_1 \cdot S_0 \cdot \bar{i} + \bar{S}_2 \cdot S_1 \cdot S_0 \cdot \bar{i} + S_2 \cdot \bar{S}_1 \cdot \bar{S}_0 \cdot \bar{i} \\ &= \bar{S}_2 \cdot \bar{S}_1 \cdot i (\bar{S}_0 + S_0) + \bar{i} (\bar{S}_2 \cdot S_1 \cdot S_0 + S_2 \cdot \bar{S}_1 \cdot \bar{S}_0) \\ &= \bar{S}_2 \cdot \bar{S}_1 \cdot i + \bar{i} (\bar{S}_2 \cdot S_1 \cdot S_0 + S_2 \cdot \bar{S}_1 \cdot \bar{S}_0) \end{aligned}$$